

9/28 - Resistor Networks

Friday, September 29, 2006

1:37 PM

weighted edge \rightarrow resistor

$$\text{Resistance} = \frac{1}{\text{weight}}$$

$$\text{conductance} = \text{weight}$$

Ohm's Law: $i(x,y)$ = current flow from x to y satisfies

$$i(x,y) = \frac{(V(x) - V(y))}{r_{x,y}} = (V(x) - V(y)) C_{x,y}$$

$$\text{so, } i(x,y) = -i(y,x)$$

Kirchoff's current law:

if node x not connected to battery,
total current flow out of $x = 0$

$$\text{i.e. } \sum_{y \sim x} i(x,y) = 0$$

Combining with Ohm's law, says



$$0 = \sum_{y \sim x} i(x,y) = \sum_{y \sim x} (V(x) - V(y)) C_{x,y}$$

$$= d_x V(x) - \sum_{y \sim x} C_{x,y} V(y)$$

$$\text{so, } V(x) = \frac{1}{d_x} \sum_{y \sim x} C_{x,y} V(y) \quad \text{where } d_x = \sum_{y \sim x} C_{x,y}$$

$V(x)$ is a weighted average of nbrs

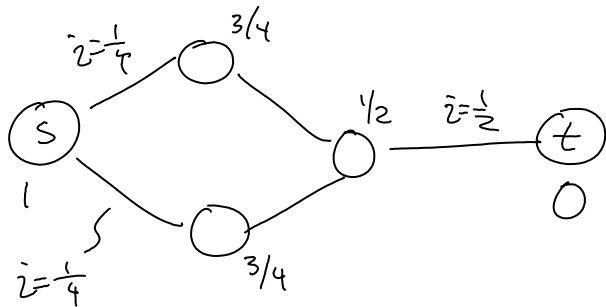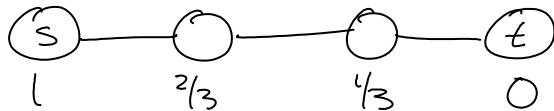Gives one equation for each non-terminal vertex.



Def $f: V \rightarrow \mathbb{R}$ is harmonic on $W \subseteq V$
if $\forall w \in W$

$$f(w) = \frac{1}{d_w} \sum_{y \sim w} C_{w,y} f(y)$$

Lemma If G is connected, $W \subset V$, $W \neq V$
and f and g are harmonic on W ,
and $\forall x \notin W$ $f(x) = g(x)$
then $f = g$

pf. Consider $h = f - g$.
Is harmonic on W .
 $h(x) = 0$ $\forall x \notin W$.

Now, let $h(z)$ be maximum.

$$\text{Then } h(z) = \sum_{y \sim z} \frac{c_{zy}}{d_z} h(y)$$

as 1. $h(y) \leq h(z)$

2. $\sum_{y \sim z} \frac{c_{zy}}{d_z} = 1$

3. $c_{zy} > 0$

we know $h(y) = h(z)$

So, by induction, for all y
reachable from z , $h(y) = h(z)$

Including $y \in U - W \Rightarrow h(z) = 0$

Similarly, can show $\min_z h(z) = 0$.

So, $h = 0$.

This implies the solution to a harmonic system
is unique.

But, do voltages exist?

Yes.

Given a graph, nodes s and t ,
want a $f: U \rightarrow \mathbb{R}$ s.t.
 $f(s) = 1$

$f(t) = 0$
 f harmonic on $V - \{s, t\}$

$\tau_{s,t}$

$F(x) = \text{Pr}[\text{a rand walk from } x \text{ hits } s \text{ before } t]$.

Clearly, $F(s) = 1$, $F(t) = 0$, and

$$F(x) = \sum_{y \sim x} \text{Pr}[\text{first step from } x \text{ to } y] F(y)$$
$$= \sum_{y \sim x} \frac{C_{xy}}{d_x} F(y)$$

So, F satisfies the equations and by uniqueness, $F = U$.

The effective conductance between s and t
is the total current flow when $V(s) = 1$, $V(t) = 0$

Let's check it's well-defined. Namely, that

$$\sum_{x \sim s} \bar{i}(s, x) = \sum_{x \sim t} i(x, t)$$

Pf.

$$0 = \sum_x \sum_{y \sim x} \tilde{i}(x, y) \quad (\text{as } \tilde{i}(x, y) = -\tilde{i}(y, x))$$

$$= \sum_{y \sim s} \tilde{i}(s, y) + \sum_{y \sim t} \tilde{i}(t, y) + \underbrace{\sum_{x \in V - \{s, t\}} \sum_y \tilde{i}(x, y)}_0$$

$$\text{so, } 0 = \sum_{y \sim s} \tilde{i}(s, y) + \sum_{y \sim t} \tilde{i}(t, y) \quad \checkmark$$

What is chance hit t before return to s ?
Denoted $\Pr\{s \rightarrow t\}$, also called
escape probability

$$= \sum_{y \sim s} \Pr\{\text{first step to } y\} \cdot (1 - F(y))$$

$$= \sum_{y \sim s} \frac{C_{s,y}}{d_s} (U(s) - U(y)) = \frac{1}{d_s} \sum_{y \sim s} \tilde{i}(s, y) = \frac{1}{d_s} C_{\text{eff}}$$

From this, can show

$$E[\# \text{ times return to } s \text{ before hit } t] = d_s R_{\text{eff}}$$

where $R_{\text{eff}} = \frac{1}{C_{\text{eff}}}$ is effective resistance

Generally, can show

$E \int_{s \rightarrow t} dx$ [times a walk starting at s hits x before t]

$$= dx \text{ Ref } U(x)$$

Finally, if flow I from s to t ,
voltages U satisfy

$$LU = (x_s - x_t)$$

$$\text{So, } U = L^+(x_s - x_t)$$

and, for any x and y , potential diff between
 x and y is $U(x) - U(y)$

$$= (x_x - x_y)^T L^+(x_s - x_t)$$

\Rightarrow Pot diff between x and y when flow I current
from s to t

= Pot diff between s and t when flow I current
from x to y